



WHEN, in the March 1966 edition, we introduced the *RCM&E Single Channel Transmitter*, we were trying to offer the non-electronically qualified novice R/C enthusiast a circuit which could be built with ease, without recourse to any special setting-up apparatus. In fact we were trying to offer a circuit which could be built and set in working order by anyone who could read and wield a soldering iron with reasonable effect.

There can be no doubt that this transmitter was a success – we still receive constant requests for photocopies of the article, since the March 1966 edition has long since been well and truly sold out. The fact that the editor's secretary is at the point of striking over the continuous photocopy requests has made the introduction of a new single channel transmitter imperative!


Some basic lessons were learned with the original circuit, most notable being that the biggest problem for constructors is the winding of the coils and construction of the centre loaded aerial. Judging from enquiries and requests for help received over the past two years, faulty coils and aerial have been the main cause of trouble, while the use of substandard or substitute transistors also accounted for a fair amount of bother.

Consequently, this new offering has been designed to use commercial, ready wound coils and aerial which should eliminate that problem, in the same way we did with the RCM&E Simpl-Simul Tx, recently published. The aerial itself has been given a considerable amount of thought. Originally we intended to use a base loaded

Simpletone

By
Rex Boyer

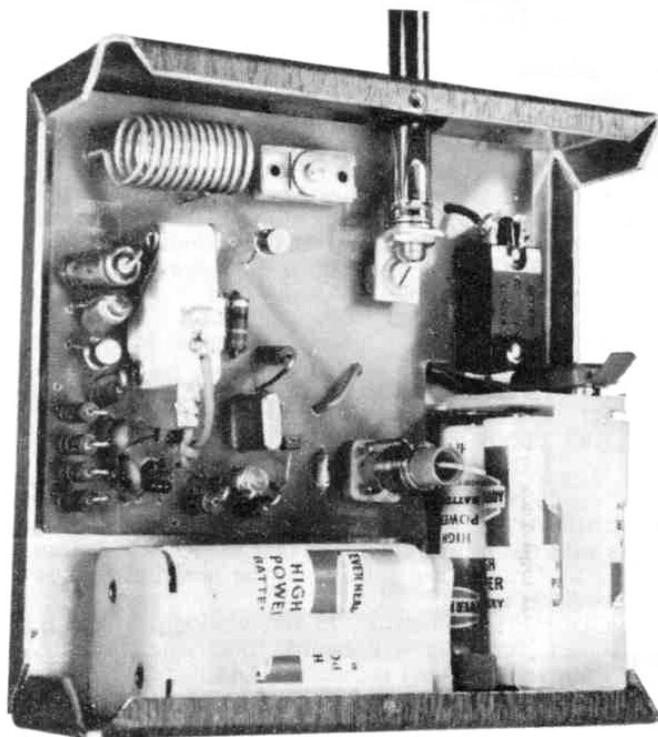A single channel tone transmitter with 'constant carrier wave' design specially for the novice R/C enthusiast



type but this would have demanded a field strength meter for setting-up, which, of course, complicates matters more than is desirable for the novice. Consequently, we have maintained the use of a centre loaded aerial which can be bought ready tuned, and the circuit now requires setting-up equipment no more technical than a small electric bulb.





We have also gone to some pains to be sure that the components, particularly transistors, are types which have manufacturer guaranteed maximum and minimum tolerances. The circuit has been designed to cope with these tolerances, and provided the specified components are used, and the circuit built as per instructions, success is assured.

Our original intention had been to develop a circuit which employed only four transistors. However, the cost of the four transistors would have been greater than that for the five now selected, so there seemed little point in using four. Three types of transistor are now used, the P346A plus the 2N4292 and 2N4290 by Piher, and each should be readily obtainable.

Components and materials

Component substitution is, as far as the average R/C enthusiast is concerned, the cardinal sin. **DO NOT ACCEPT ANY COMPONENT SUBSTITUTIONS**

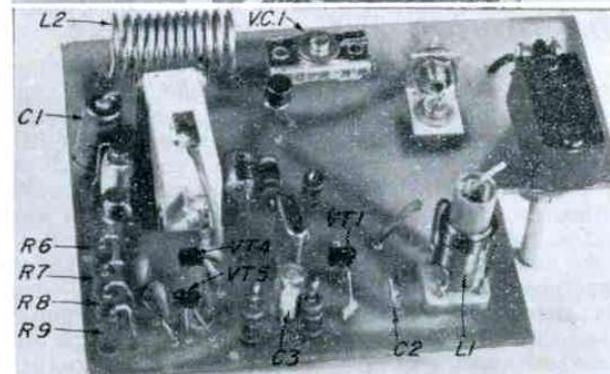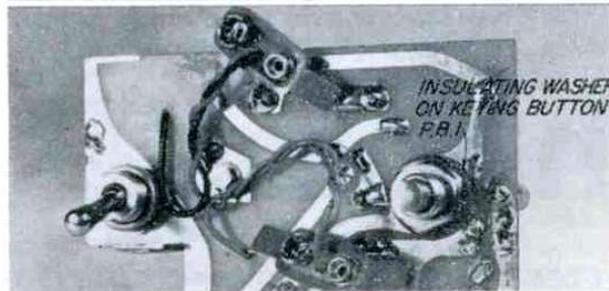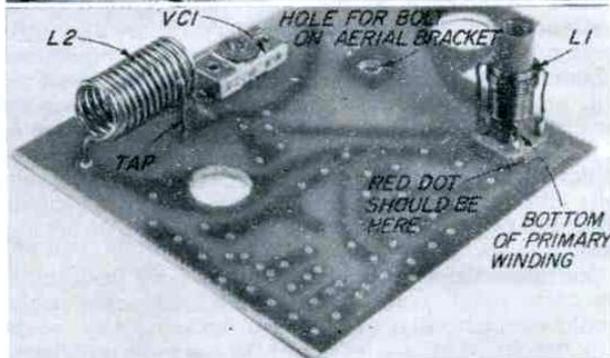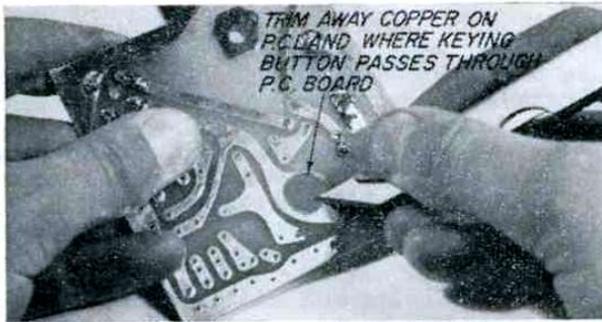Top: prototype Simpletone transmitter, with case covered in wood grain Fablon. MonoKote would be a good alternative covering. Left: rear of case removed to reveal internal layout and battery clips.



Top: remove copper from around hole where keying button P.B.1. passes through, to prevent neck shorting on copper. Second down: Coil identification, showing tap on P.A. coil and bottom of primary winding on oscillator coil. Orientate oscillator coil as shown. Third down: view of copper side of p.c. board identifying insulating washer on keying button P.B.1. Above: general view of component layout. Note solder tags on keying button.

whatsoever, no matter how technically qualified your adviser may be.

If you are going to make your own pc board you can take a print from the full size illustration Fig. 4. If, on the other hand you buy a ready drilled and etched circuit board, we strongly suggest you check to make sure it is made of 1/16 in glass fibre. This is important because the aerial is supported on the pc board and we found the paper type of board just did not stand up to general wear and tear in this respect. The glass fibre board also has far better insulative properties and is therefore doubly desirable.

Assembly of P.C. Board

Start assembly by making sure the keying button and switch pass through their respective holes in the pc board. Be sure also that the copper around the hole through which the neck of the keying button passes is relieved to prevent the copper land from shorting out onto the button (see photograph). The retainer nut for the keying button should be insulated from the lands by an insulative washer. The on/off switch however, should make good contact with the pc board as this earths the live rail to the case.

Tick off the components as you solder them into the board by placing your "job done" mark in the brackets by each assembly stage instructions.

Coils

The first parts to be put on the board are the coils. Refer to Fig. 2 and photographs opposite.

- () Oscillator coil (L1) Teleradio type 88/0. Solder in position using the red dot for orientation. Before doing so however, check to see that the red dot is adjacent to the correct pin, which should be the one which connects to the bottom of the primary winding (the longest winding wound up against the body of the coil former). See photograph for clarifications.
- () PA coil (L2) Teleradio type 88/PA. This should have the ends cleaned. However, if as is likely, you have a coil with enamelled wire you will have to use a modelling knife to bare the wire to within $\frac{1}{8}$ in of the coil windings. If you have a tinned copper coil you only have to clean the ends and the taping lead. Push the coil into its holes. You will notice the hole spacing is such that the coil will be expanded when finally fixed in position. To position the coil correctly, take a piece of $\frac{1}{8}$ in scrap balsa and place between the board and the coil, to obtain the necessary stand off distance. Press the coil down onto the balsa and cut off the leads $\frac{3}{16}$ in long on the copper side of the board. Bend the leads over to lay flat on the board and with an assistant to hold the coil in place, solder. Then space out evenly.

Resistors

Take all resistors (10 per cent tolerance, $\frac{1}{2}$ watt) and thoroughly clean the leads by drawing them through a slit in a rubber eraser so that the solder will take easily. Referring to Fig. 2, solder as follows identifying by coloured band sequence indicated below. Note that the first three colour bands are mentioned, the fourth will be the silver 10 per cent tolerance indication.


- () R1 47K Ω Yellow Mauve Orange Vertical
- () R2 4.7K Ω Yellow Mauve Red Vertical
- () R3 330 Ω Orange Orange Brown Vertical
- () R4 27 Ω Red Mauve Black Horizontal
- () R5 2.2K Ω Red Red Red Vertical
- () R6 1.5K Ω Brown Green Red Vertical
- () R7 22K Ω Red Red Orange Vertical
- () R8 22K Ω Red Red Orange Vertical
- () R9 1.5K Ω Brown Green Red Vertical

Capacitors

As with the resistors, be sure that the leads are clean before soldering. Then solder into the board as follows referring to Fig. 2:

- () C1: 25 μ F electrolytic, 25 volt working (Mullard). Insert vertically on board, observing polarity. Positive (+ve) end is 'waisted' and there is a black insulator in the end where the +ve lead protrudes (see Fig. 3). Capacitor stands vertically on -ve end with +ve end uppermost.

Fig. 1: Theoretical circuit

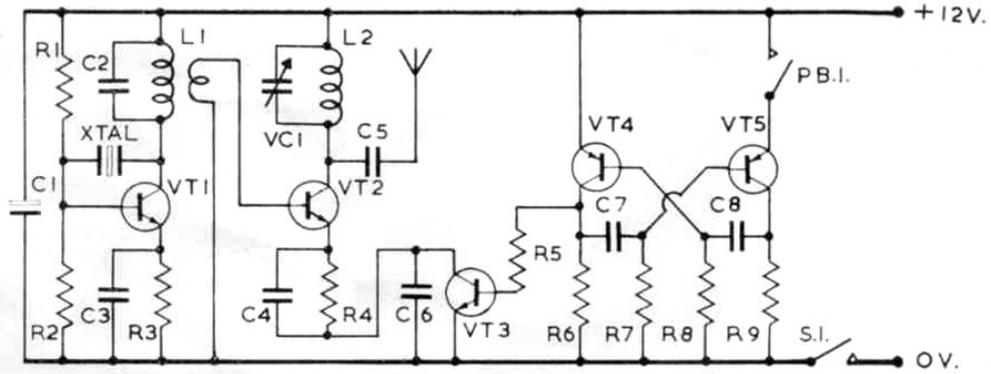


Component values

R1 : 47K Ω	C2 : 22pF Radiospares	VT4 : 2N4290 Piher (supplied in G.B. by Waycomb)	P.B.I. (Keying button)
R2 : 4.7K Ω	C3 : 1000 pF Radiospares	VT5 : 2N4290 Piher (supplied in G.B. by Waycomb)	: Micro Push Button.
R3 : 330 Ω	C4 : 1000 pF Radiospares	VC1 : 140 pF Radiospares	: MacGregor Industries or Radiospares
R4 : 27 Ω	C5 : 1000 pF Radiospares	XTal : 3rd Overtone Miniature, 27 MHz band	Aerial : D. Olley or Horizon Systems
R5 : 2.2K Ω	C6 : 1000 pF Radiospares	S1 : Radiospares Light Duty S.P.S.T.	L1 : Teleradio type 88/0
R6 : 1.5K Ω	C7 : 47K pF Radiospares		L2 : Teleradio type 88/PA
R7 : 22K Ω	C8 : 47K pF Radiospares		Case : 20 s.w.g. Aluminium
R8 : 22K Ω	Disc Ceramics		
R9 : 1.5K Ω	Disc Ceramics		




All resistors $\frac{1}{2}$ watt 10 per cent Radiospares
 C1 : 25 μ F 25v. electrolytic Mullard.

Fig. 2: Component placement diagram

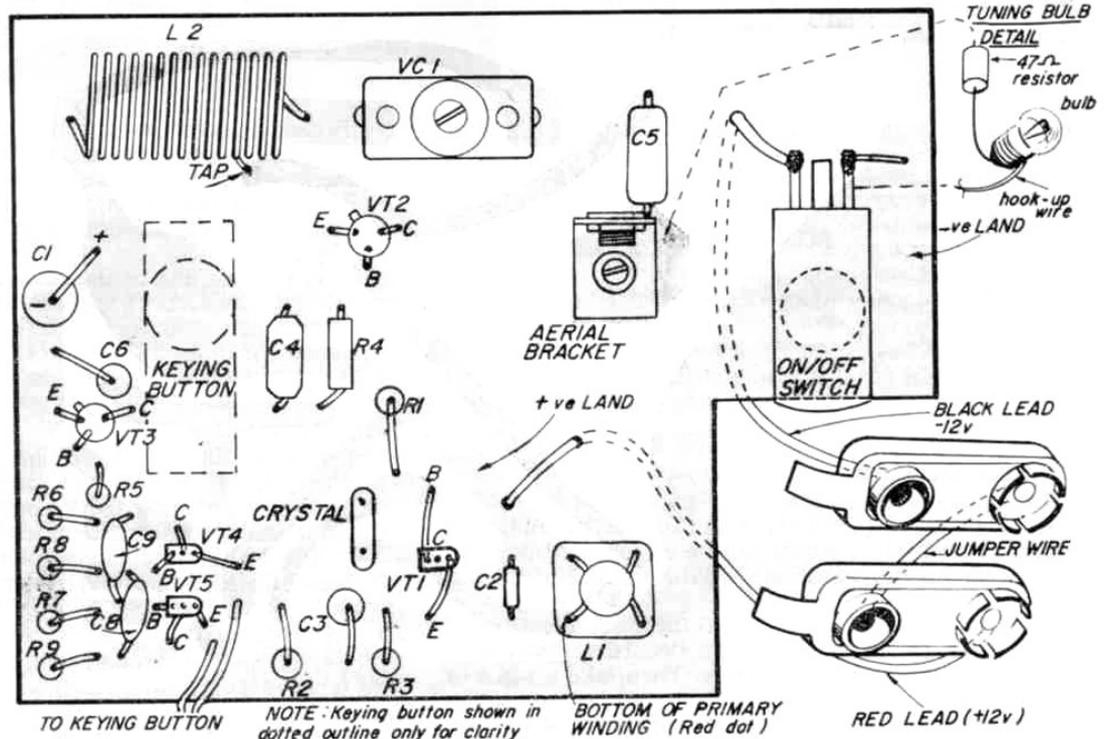

Note: tuning bulb, top right is removed after tuning operation

Fig. 3: lead identifications for transistors and capacitors C1

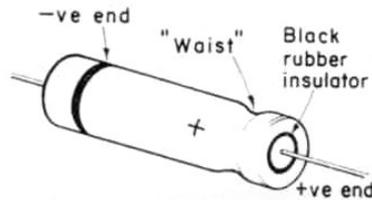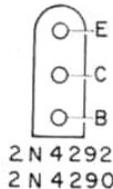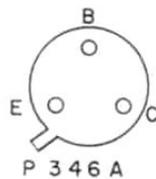


() C2: 22pf Radiospares	Polystyrene	Horizontal
() C3: 1000pf Radiospares	Polystyrene	Vertical
() C4: 1000pf Radiospares	Polystyrene	Horizontal
() C5: 1000pf Radiospares	Polystyrene	Horizontal
() C6: 1000pf Radiospares	Polystyrene	Vertical
() C7: 47K pf Radiospares	disc. ceramic	Vertical
() C8: 47K pf Radiospares	disc. ceramic	Vertical

Transistors

Refer to Fig. 3 for corrected identification of emitter (e), collector (c) and base (b) connection which *must* be observed.

Then solder in transistors as follows (referring to Fig. 2), using a heat shunt on each lead as it is soldered,

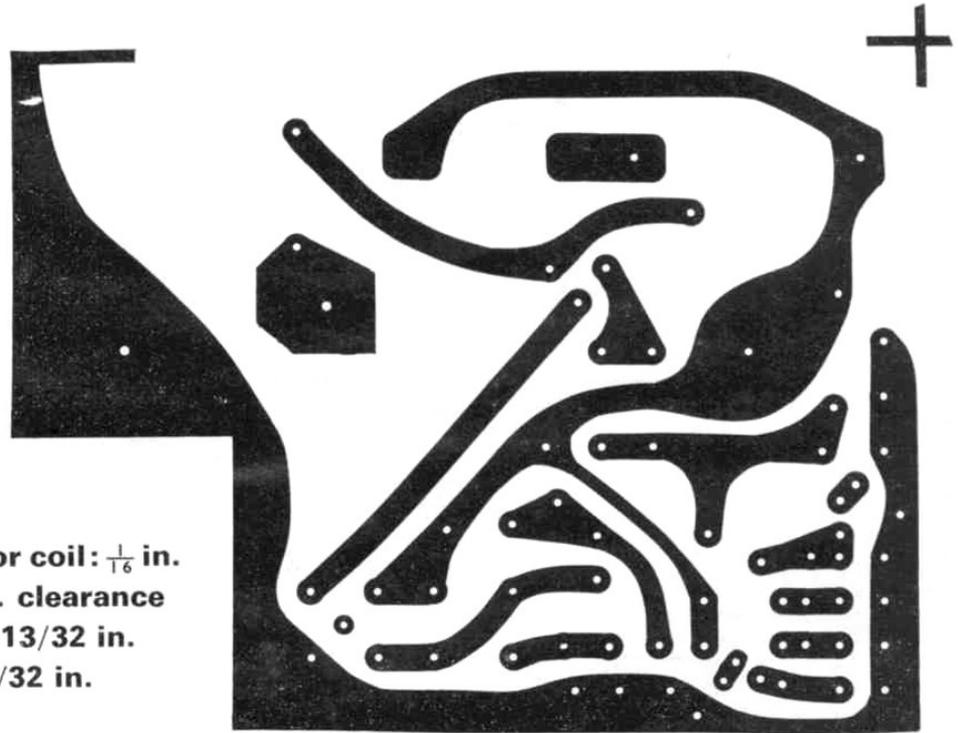Fig. 4**Printed Circuit layout****Drilling details:****Small holes: 1 mm.****P. A. coil and oscillator coil: $\frac{1}{16}$ in.****Aerial bracket: 6 B. A. clearance****Keying Button P.R.I.: $\frac{13}{32}$ in.****On/off switch S.1: $\frac{15}{32}$ in.****VC1: $\frac{1}{8}$ in.**

so that no damage is done to the transistor. If a proper heat shunt tool is not available, use a pair of tweezers, gripping the lead to dissipate the heat.

- () VT1: 2N4292 Piher
- () VT2: P346A
- () VT3: P346A SGS Fairchild
- () VT4: 2N4290 Piher
- () VT5: 2N4290 Piher

Crystal (Xtal)

- () The crystal (xtal) is also a delicate component and the leads to this should also be heat shunted when soldering. (See Fig. 2).

On/off Switch

The on/off switch S1 is a Radiospares, light duty single pole, single throw (SPST) type and the Keying Button is a micro action type, which can be obtained from MacGregor Industries, Station Wharf, Langley, Bucks., price 9s. 6d.

- () Fit the on/off switch S1 onto the component board with its solder tags pointing toward the top edge (longest side). Tighten firmly. Then take a piece of excess wire lead from one of the resistors and solder from the tag facing the outer edge of the board into the -ve land just below this tag. The -ve land is the one which passes round the edge on three sides of the board, and is identified on Fig. 2.
- () To the other tag on S1, solder a 9 in length of *Black* 14/.0076 hook-up wire and pass this through the supporting hole above and to the left of this tag.

Keying Button

- () The keying button must not short on any of the copper pc lands, so check again that the neck of the button does not short on the copper where it passes through the board, referring once again to the photograph showing how the copper is carved away from the periphery of the hole.

Fit onto the board and tighten into position, insulating the nut from the copper lands with an insulative washer.

- () Take two short lengths of 14/.0076 *Red* hook-up wire and solder, one each to the two solder tags on the keying button. Take the free end of one lead (it does not matter which), bare the end and solder into the unused hole adjacent to the emitter of VT5. (see Fig. 2).
- () Bare the free end of the remaining wire and solder into hole adjacent to the emitter of VT4 in the +ve land. Again refer to Fig. 2.
- () Solder a 9 in length of red 14/.0076 hook-up wire to the +ve land as indicated in Fig. 2.

Checking

- () Before you connect the circuit up to a battery, check every detail of the work completed so far. Pay particular attention to the orientation of the transistor leads, coils and the electrolytic capacitor C1. Also be sure that none of the copper lands have been bridged with excess solder.

Aerial Bracket

The aerial bracket should be constructed as per Fig. 5. Two types of aerial can be used with this transmitter, the D. A. Olley Fleet Aerial or the Horizon Systems aerial. Each works well and can be obtained ready tuned, provided that a specific frequency is requested. Mount the aerial bracket using a 6 BA bolt and nut.

Batteries and wiring up

This circuit works off a 12 volt power supply, comprising eight pen cells. For convenience we have used two plastic type battery clips for these. Connections to the batteries are effected by small battery clips and the wiring system can be found in Fig. 2.

Tuning up

The beauty of this circuit is that it requires no expensive setting-up equipment. This did not just 'occur' of course, we designed it specifically for the novice who cannot afford to pay more for a test meter than he does for his transmitter.

